

University of Porto

Department of Electrical and Computer Engineering



Universidade do Porto

Faculdade de Engenharia

FEUP

Raport Lab 1

Subtitle or Course Code

Prepared by:

Carolina Fernandes

Student ID: 202208842

Email: up202208842@fe.up.pt

Michał Dzikowski

Student ID: 202500461

Email: up202500461@fe.up.pt

José Martinez-Cattáneo Roy

Student ID: 202502861

Email: up202502861@edu.fe.up.pt

October 20, 2025

Abstract

This is the abstract of your report. Provide a brief summary of the main points, methodology, findings, and conclusions of your report. Keep it concise and informative—typically 150–300 words.

Contents

1	Introduction	2
1.1	Background	3
1.2	Base Calculated Parameters	3
1.3	Objectives	4
2	First Simulation Results	5
2.1	Simulation Setup Task 1.A	5
2.2	Task 1.B	6
2.3	Task 1C	7
2.4	Task 1D	7
2.5	Task 1E	8
2.6	Task 1F	9
3	Simulation Task 2	10
3.1	Task 2A	10
3.2	Task 2B	10
3.3	Task 2C	11
4	Results and Discussion	12
4.1	Results	12
4.2	Discussion	12
5	Conclusion	13
5.1	Summary	13
5.2	Future Work	13

Chapter 1

Introduction

This report analyzes the performance and characteristics of a three-phase, Y-connected induction machine under non-sinusoidal supply conditions. The system under consideration is specified as follows:

- **Rated Power:** 500 kW
- **Line-to-Line Voltage:** 2300 V
- **Frequency:** 60 Hz
- **Number of Poles:** 4
- **Connection:** Three-phase, Y-connected

The equivalent circuit parameters of the induction machine are:

- Stator resistance (R_s): 0.12Ω
- Rotor resistance (R_r): 0.32Ω
- Stator leakage reactance (X_{ls}): 1.4Ω
- Rotor leakage reactance (X_{lr}): 1.3Ω
- Magnetizing reactance (X_M): 47.2Ω

The combined moment of inertia of the machine shaft and its load is $11.5 \text{ kg}\cdot\text{m}^2$. The damping coefficient (B) is assumed to be negligible for the purposes of this analysis.

The induction motor is supplied by a voltage-sourced inverter (VSI), which provides non-sinusoidal voltage waveforms. A schematic representation of the VSI feeding the induction motor is shown in the figure below.

1.1 Background

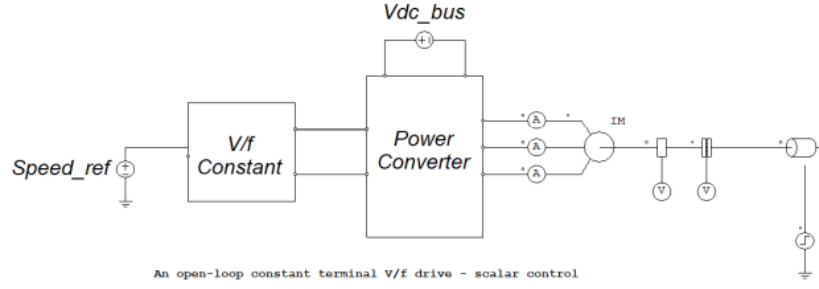


Figure 1.1: Overview of the simulated induction machine system.

1.2 Base Calculated Parameters

Based on the machine data provided in the introduction, the following base parameters can be calculated:

- **Base Apparent Power (S_{base}):** 500 kVA (using rated power)
- **Base Line-to-Line Voltage ($V_{LL,base}$):** 2300 V
- **Base Phase Voltage ($V_{ph,base}$):**

$$V_{ph,base} = \frac{V_{LL,base}}{\sqrt{3}} = \frac{2300}{\sqrt{3}} \approx 1327 \text{ V}$$

- **Base Current (I_{base}):**

$$I_{base} = \frac{S_{base}}{\sqrt{3} \cdot V_{LL,base}} = \frac{500\,000}{\sqrt{3} \times 2300} \approx 125.5 \text{ A}$$

- **Base Impedance (Z_{base}):**

$$Z_{base} = \frac{V_{ph,base}}{I_{base}} = \frac{1327}{125.5} \approx 10.58 \text{ } \Omega$$

- **Base Angular Frequency (ω_{base}):**

$$\omega_{base} = 2\pi f = 2\pi \times 60 \approx 377 \text{ rad/s}$$

- **Base Synchronous Speed (n_{sync}):**

$$n_{sync} = \frac{120 \times f}{P} = \frac{120 \times 60}{4} = 1800 \text{ rpm}$$

- **Base Torque (T_{base}):**

$$T_{base} = \frac{P_{base}}{\omega_{sync}} = \frac{500\,000}{377} \approx 1326 \text{ Nm}$$

These base values are useful for per-unit system calculations and for analyzing the performance of the induction machine. Provide relevant background information about your topic.

1.3 Objectives

State the main objectives of your report.

Chapter 2

First Simulation Results

2.1 Simulation Setup Task 1.A

This is bridge design on the perfect switches that is able to convert from DC to AC

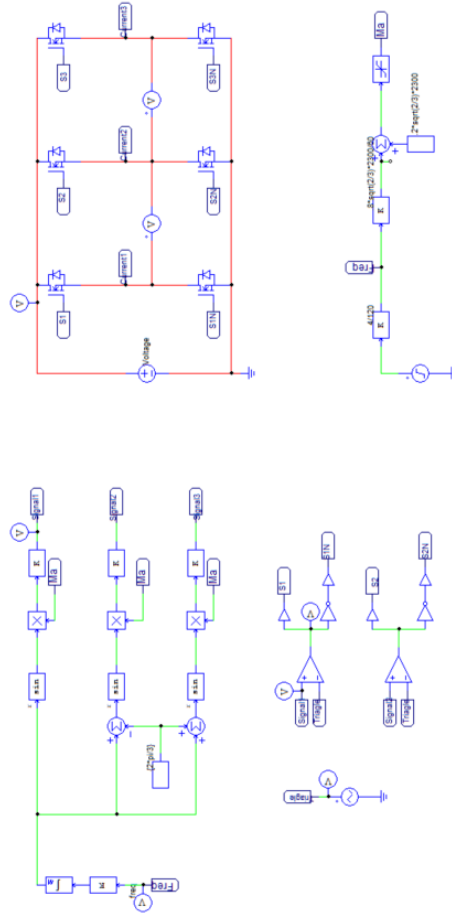


Figure 2.1: The simulation setup for Task 1a, illustrating the main components and connections used in the analysis. The layout allows for a clear understanding of the system configuration and the relationships between the inverter, induction machine, and measurement points.

2.2 Task 1.B

To obtain the nominal line-to-line RMS voltage ($V_{LL,rms}$) of the motor at the fundamental harmonic, the minimum DC bus voltage ($V_{DC,min}$) for a three-phase inverter can be calculated as follows:

$$V_{PH,peak} = \frac{ma \cdot V_{DC,min}}{2} \quad (2.1)$$

$$V_{LL,rms} = \frac{ma \cdot V_{DC,min}}{2 \cdot \sqrt{2}} \quad (2.2)$$

$$V_{DC,min} = \frac{V_{LL,rms}}{0.612} \quad (2.3)$$

$$V_{DC,min} \approx 3700 \text{ V} \quad (2.4)$$

Second part of the task consist of choosing the right modulation frequency (f_{mod}) and switching frequency ($f_{carrier}$).

$$f_{mod} = 60 \text{ Hz} \quad (2.5)$$

$$f_{carrier} = 3000 \text{ Hz} \quad (2.6)$$

$$m_f = \frac{f_{carrier}}{f_{mod}} = \frac{3000}{60} = 50 \quad (2.7)$$

Depending on the modulation index (ma) the total harmonic distortion (THD) will change. For this task we have chosen $ma = 0.8$ which gives us $THD = 21.13\%$. Also modulation index affects the RMS voltage delivered to the motor. Mf in range of 30 - 50 is acceptable, provides good compromise between switching losses and harmonic distortion. Mf in range of 60 – 100 provides lower harmonic distortion but increases switching losses. While values above 100 are not recommended due to high switching losses and high simulation strain.


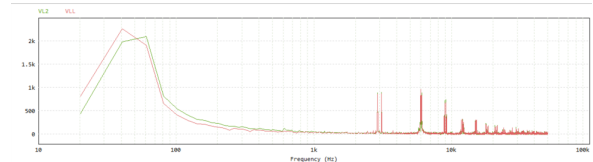
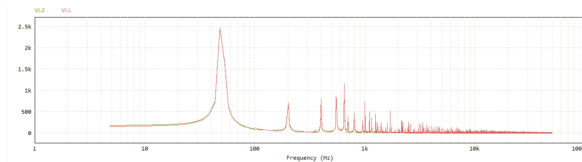


Figure 2.2: FFT of carrier wave at 300 Hz

Figure 2.3: FFT of carrier wave at 3000 Hz

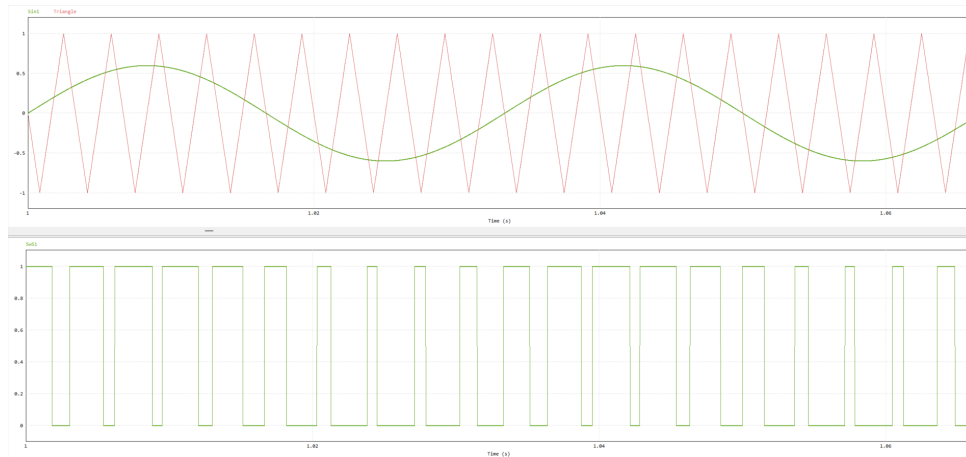2.3 Task 1C

To illustrate PWM operation, we were required to present the inverters behavior during a full period of the 30Hz reference (control) wave. This included showing both the reference signal and the corresponding command signals for the switches. The resulting waveforms demonstrate how PWM modulates the switching states to achieve the desired output voltage.



2.4 Task 1D

In this task we visualized current and voltage waveforms when motor operates at 1200 rpm which gives 40 Hz.

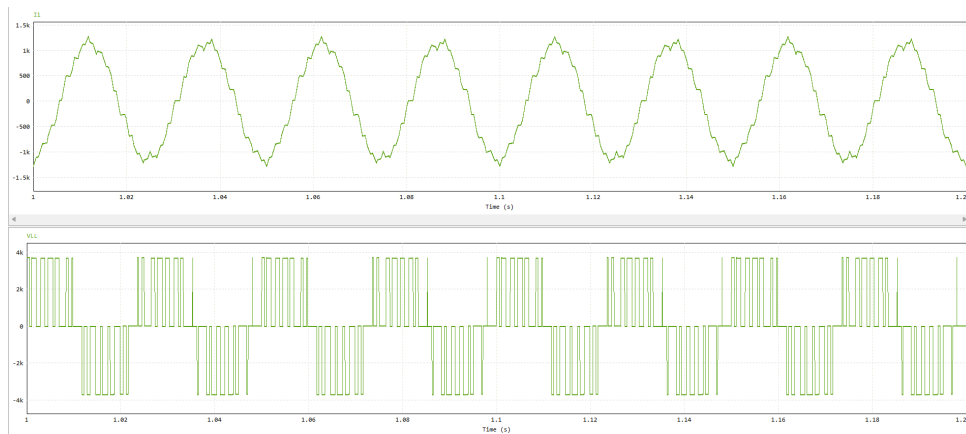


Figure 2.4: Voltage and Current waveforms at 1200 rpm (40 Hz).

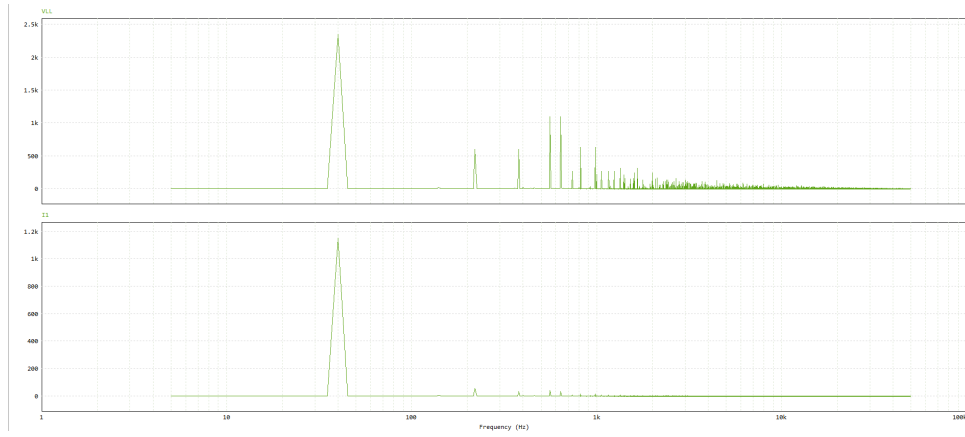


Figure 2.5: FFT of phase A current at 1200 rpm (40 Hz).

X	THD of I_1	THD of V_{LL1}
40 Hz Carrier	0.075 %	0.99 %

Table 2.1: Total Harmonic Distortion (THD) values for I_1 and V_{LL1} at different carrier frequencies.

One step inverter operates with high harmonic distortion. Switches operate between V_{dc} and 0V. This causes high THD values in voltage and current waveforms. THD can be reduced by using multilevel inverters.

2.5 Task 1E

Using the simulation setup from Task 1.A, we analyzed the induction machine's performance under load conditions with open loop control. This was a behavior of the machine.

- At time $t = 0 - 1.5s$, the machine was supposed to achieve 500 rpm speed without load.
- At time $t = 1.5s$, machine was set up to 1000 rpm speed without load.
- At time $t = 3.5s$, a load torque of 2500 Nm was applied.

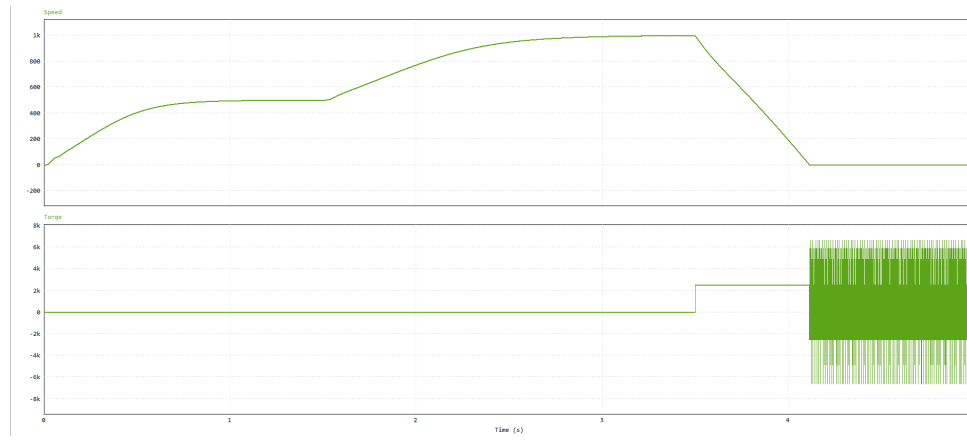


Figure 2.6: Speed and Torque response of the induction machine under specified load conditions.

2.6 Task 1F

Chapter 3

Simulation Task 2

3.1 Task 2A

3.2 Task 2B

Using Thevenin equivalent to model the induction machine. We were able to simplify the analysis of the machine's behavior under various operating conditions. And create MatLab scripts to calculate Torque under different slip values for given frequency.

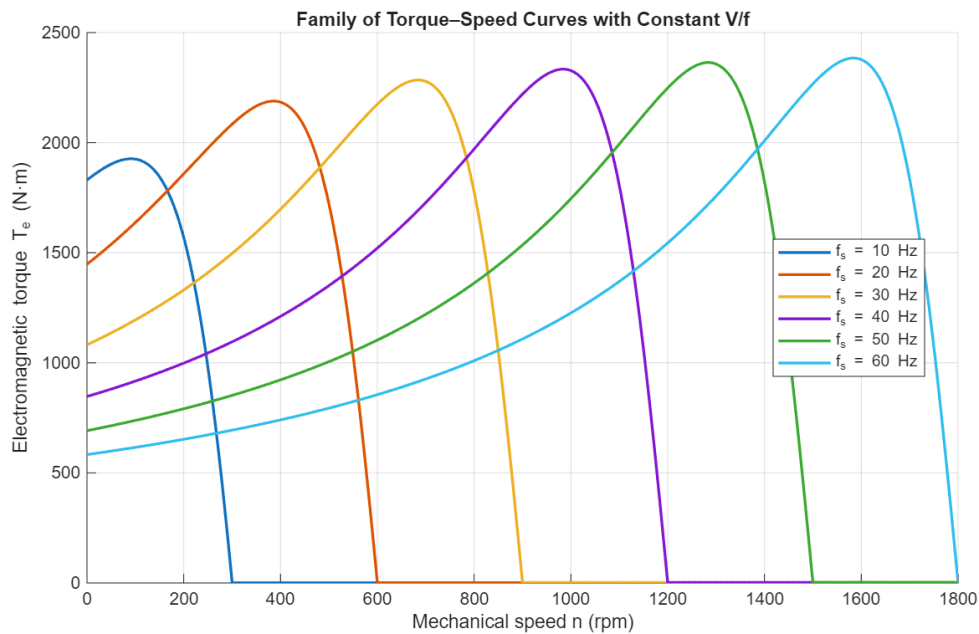


Figure 3.1: Torque vs Slip curve for the induction machine using Thevenin equivalent model.

3.3 Task 2C

In this task our objective was to introduce closed loop control with speed reference. It was achieved by subcreating the speed error and feeding it to a P controller shown in the figure 3.2. This simple control unfortunately was not able to provide satisfactory results. As presented in the figure 3.3, the speed is not able to reach the reference value. Values of the error signal and modulation are shown in the figure 3.4 where it is clear we are operating within saturation limits.

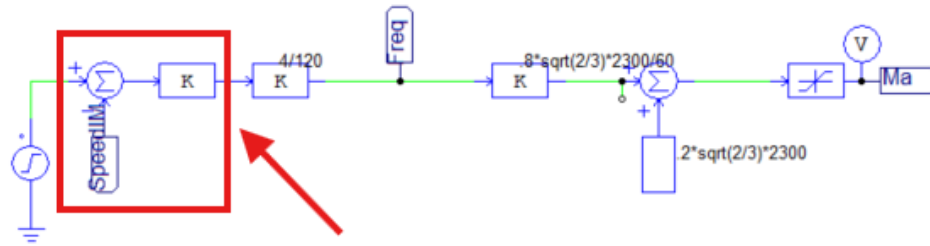


Figure 3.2: Closed loop control with speed reference.

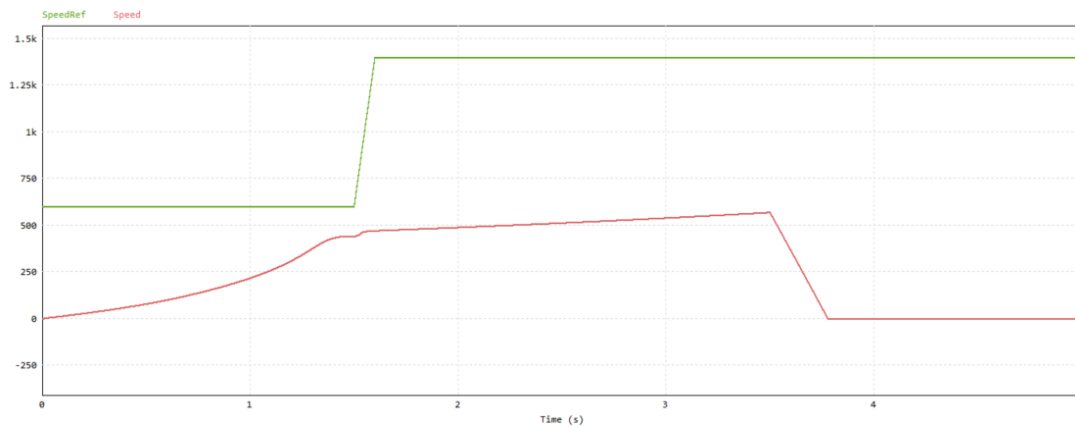


Figure 3.3: Speed and reference tracking with closed loop control.

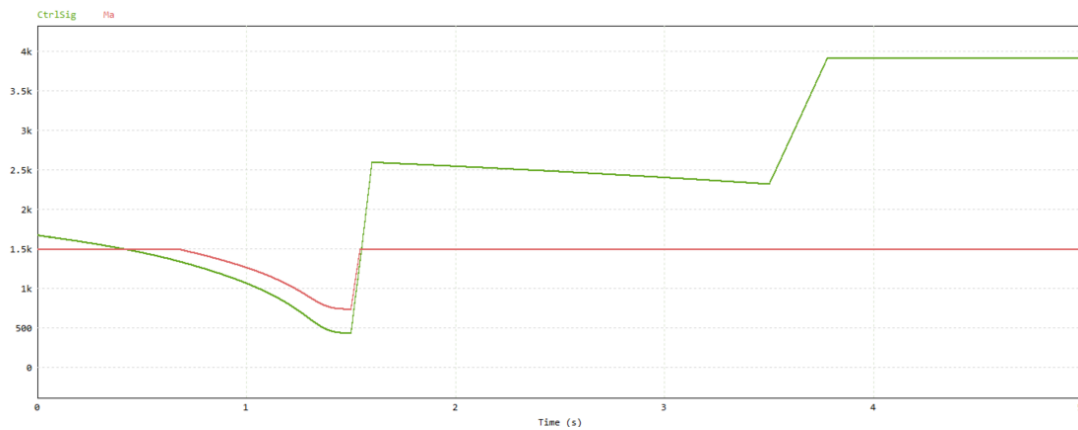


Figure 3.4: Ma with error signal in closed loop control.

Chapter 4

Results and Discussion

Present your results and discuss their implications.

4.1 Results

Present your findings here.

4.2 Discussion

Discuss the implications of your results.

Chapter 5

Conclusion

Summarize your findings and provide concluding remarks.

5.1 Summary

Provide a summary of your work.

5.2 Future Work

Suggest areas for future research or development.